



I had one of these to repair at the same time some questions were asked about it on Aron's forum on Ampage, so I traced out the circuit.

Most details should be right with this version of the drawing. Before giving the fixed unit back I had one last look at the resistors in daylight to get the right colour codes, so I'm pretty sure they're ok now.

The transistor number I originally thought was used is a T03 cased power transistor according to the list Paul Perry looked at, so I'm going with the 2N5088 for now.

Having said that everything here is unverified so we'll have to wait for somebody to build one to see if it works!

Mike Matthews / New Sensor Corp.

# Soul Kiss

Drawing: Steve Newton  
Date: 9 November 2001