



Fig. 3. Circuit diagram of the enhancer (to the right of the dashed line), and the impedance inverter for use with guitars.