



IC1 = NE5534AN
 A1; A2 = IC3 = TL072

Fig. 3. Circuit diagram of the enhancer (to the right of the dashed line), and the impedance inverter for use with guitars.