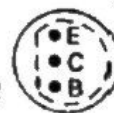


BASS BRASS MASTER MODEL BB-1


Original Schematic modified for clarity (Twin -T filter) and annotated to match Geofex PCB layout of the circuit.

BASING DIAGRAMS
TOP VIEWS

All Transistors
except Q6 - 2N3392



2N5308
Q6

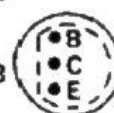

Quirks:

1. There really ought to be input and output pull down resistors (1M)
2. Bass Volume and Brass Volume can be separate pots or dual linear wired as blend.
3. T1's original specs are unknown. A Mouser 10Kct to 10Kct audio transformer should work fine.
4. The Millenium Bypass should work fine - See GEOFEX for details.

