
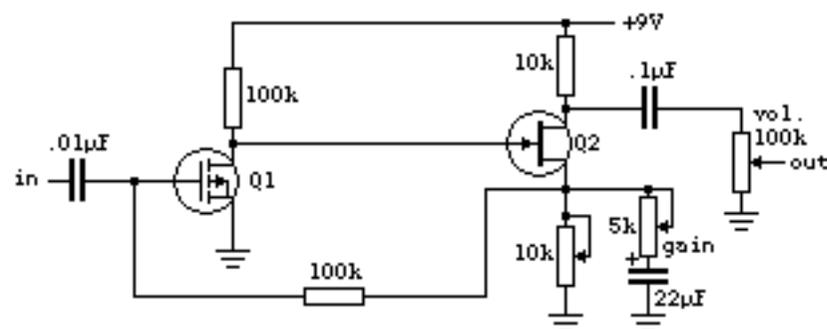



*Circuit A*

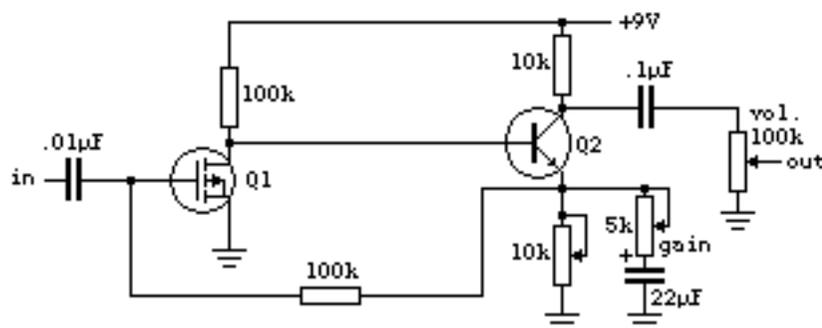


*Circuit D*



*Circuit B*

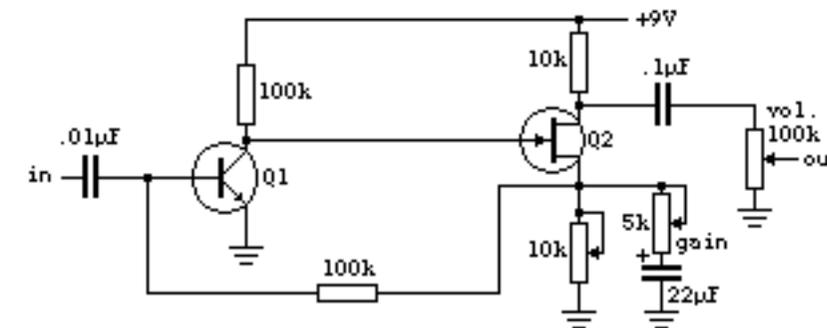

*Circuit E*

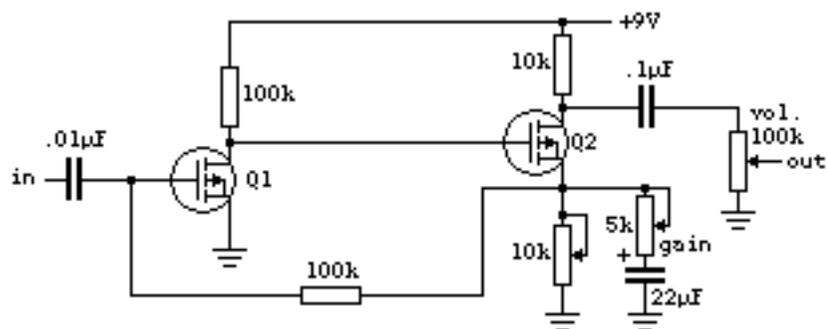

*Circuit C*

The 10k source/emitter trimpot on Q2 allows many transistors to be plugged in without changing any other components. Simply adjust it until you find a setting that pleases.

Mosfet can be 2N7000, 2N7007

JFET tried was a 2N3819

BJT can be just about anything-2N3904, MP5A18, NTE103A(Germanium), MP5A14 (Darlington)...all work.