



This circuit converts the guitar signal to a variable duty cycle pulse wave. The 500k pot controls the pulse width and can be put under control of a LFO, envelope follower, or external CV. Making for radical and animated waveform transformation, in the vein of analog synthesizers.